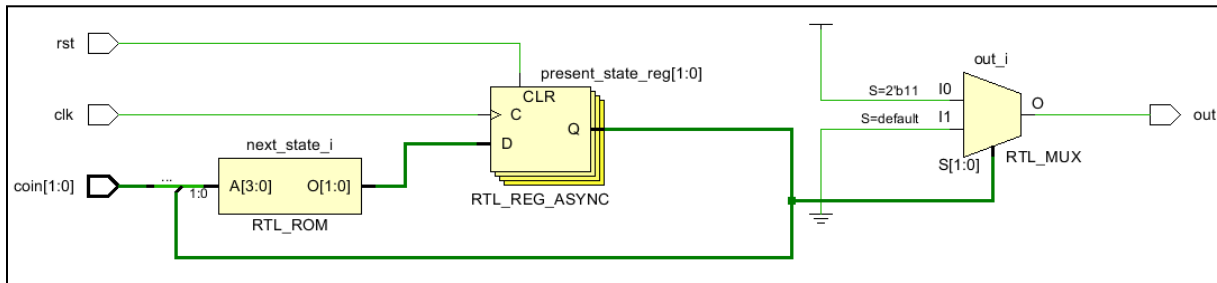


DSD LAB SESSION 6

Design and simulate the Vending Machine FSM using behavioral modeling in Verilog HDL

Moore Implementation Verilog Code

```
module moore(  
    input clk, rst,  
    input [1:0] coin, //00 = 0 cent, 01 = 5 cents, 10 = 10 cents  
    output reg out);  
localparam S0 = 2'b00, S5 = 2'b01, S10 = 2'b10, S15 = 2'b11 ;  
reg [1:0] present_state, next_state;  
//NEXT STATE COMBINATIONAL LOGIC (Depends upon Present State and Inputs)  
always @ (*) begin  
    casez ({coin,present_state})  
        {2'b00,S0}: next_state = S0;  
        {2'b01,S0}, {2'b00,S5}: next_state = S5;  
        {2'b10,S0}, {2'b01,S5}, {2'b00,S10}: next_state = S10;  
        {2'b10,S5}, {2'b01,S10}, {2'b10,S10}: next_state = S15;  
        default: next_state = S0;  
    endcase  
end  
// STATE REGISTER SEQUENTIAL LOGIC  
always @ (posedge clk or posedge rst) begin  
    if (rst) present_state <= S0;  
    else present_state <= next_state;  
end  
//OUTPUT COMBINATIONAL LOGIC  
always @(present_state) begin  
    case (present_state)  
        S15: out = 1'b1;  
        default: out = 1'b0;  
    endcase  
end  
endmodule
```




Moore Implementation Testbench

```
`timescale 1ns/1ps  
module tb_moore;  
    // Testbench signals  
    reg clk, rst;  
    reg [1:0] coin; // 00 = 0¢, 01 = 5¢, 10 = 10¢  
    wire out;  
    // Instantiate DUT (Device Under Test)  
    moore uut (  
        .clk(clk), .rst(rst), .coin(coin), .out(out)  
    );  
    // Clock generation: 10 ns period (100 MHz)  
    always #5 clk = ~clk;  
    // Test sequence  
    initial begin  
        // Initialize
```

```

clk = 0; rst = 1; coin = 2'b00;
// Apply reset for one cycle
@(posedge clk);
rst = 0;
// === Test 1: Insert 5¢ + 10¢ → should output 1 at 15¢ ===
@(posedge clk); coin = 2'b01; // insert 5¢
@(posedge clk); coin = 2'b00; // no coin
@(posedge clk); coin = 2'b10; // insert 10¢
@(posedge clk); coin = 2'b00; // FSM should output 1 here
// === Test 2: Insert 10¢ + 10¢ → output should pulse again ===
repeat(2) @(posedge clk); // wait a couple cycles
coin = 2'b10; // insert 10¢
@(posedge clk); coin = 2'b10; // another 10¢ (total 20¢)
@(posedge clk); coin = 2'b00; // FSM resets after dispensing
// === Test 3: Insert 5¢ + 5¢ + 5¢ ===
repeat(2) @(posedge clk);
coin = 2'b01; @(posedge clk);
coin = 2'b01; @(posedge clk);
coin = 2'b01; @(posedge clk); // total 15¢ now
coin = 2'b00; @(posedge clk);
// Finish simulation after a few more cycles
repeat(5) @(posedge clk);
$finish; end endmodule

```

 

Mealy Implementation Verilog Code:

```


module mealy(
    input clk, rst,
    input [1:0] coin, //00 = 0 cent, 01 = 5 cents, 10 = 10 cents
    output reg out);
localparam S0 = 2'b00, S5 = 2'b01, S10 = 2'b10;
reg [1:0] present_state, next_state;
//OUTPUT LOGIC & NEXT STATE COMBINATIONAL LOGIC (Both depend upon Present State and Inputs)
always @ (*) begin
    casez ({coin,present_state})
        {2'b00,S0}: begin
            next_state = S0; out = 0;
        end
        {2'b01,S0}, {2'b00,S5} : begin
            next_state = S5; out = 0;
        end
        {2'b10,S0}, {2'b01,S5}, {2'b00,S10} : begin
            next_state = S10; out = 0;
        end
        {2'b10,S5}, {2'b01,S10}, {2'b10,S10}: begin
            next_state = S0; out = 1;
        end
        default: begin
            next_state = S0; out = 0;
        end
    endcase
end
// STATE REGISTER SEQUENTIAL LOGIC
always @ (posedge clk or posedge rst) begin

```

```

    if (rst) present_state <= S0;
    else present_state <= next_state;
end
endmodule

```

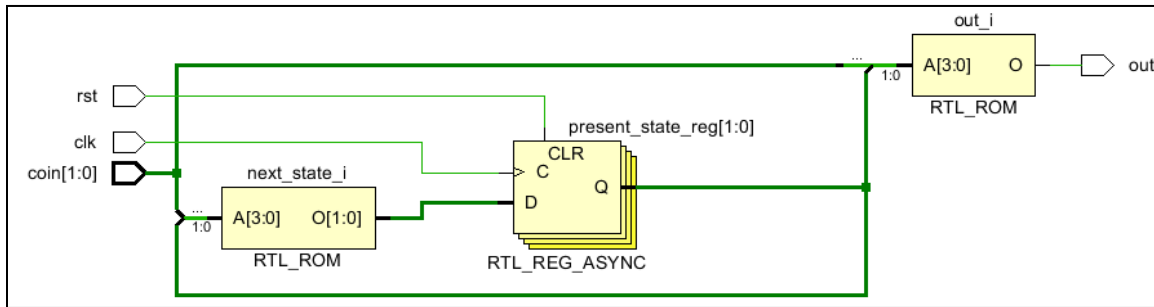

```

`timescale 1ns/1ns
module tb_mealy;
    // Testbench signals
    reg clk, rst;
    reg [1:0] coin;    // 00 = 0¢, 01 = 5¢, 10 = 10¢
    wire out;
    // Instantiate DUT (Device Under Test)
    mealy uut (.clk(clk), .rst(rst), .coin(coin), .out(out));
    // Clock generation: 10 ns period (100 MHz)
    always #5 clk = ~clk;
    // Test sequence
    initial begin
        // Initialize
        clk = 0; rst = 1; coin = 2'b00;
        // Apply reset for one cycle
        @(posedge clk);
        rst = 0;
        // === Test 1: 5¢ + 10¢ → should output 1 when total reaches 15¢ ===
        @(posedge clk); coin = 2'b01;    // Insert 5¢
        @(posedge clk); coin = 2'b00;    // No coin
        @(posedge clk); coin = 2'b10;    // Insert 10¢ (expect out=1 here, Mealy)
        @(posedge clk); coin = 2'b00;    // No coin
        // === Test 2: 10¢ + 10¢ ===
        repeat(2) @(posedge clk);
        coin = 2'b10; @(posedge clk);    // Insert 10¢
        coin = 2'b10; @(posedge clk);    // Another 10¢ (expect out=1)
        coin = 2'b00; @(posedge clk);    // No coin
        // === Test 3: 5¢ + 5¢ + 5¢ ===
        repeat(2) @(posedge clk);
        coin = 2'b01; @(posedge clk);    // 5¢
        coin = 2'b01; @(posedge clk);    // 10¢ total
        coin = 2'b01; @(posedge clk);    // 15¢ (expect out=1)
        coin = 2'b00; @(posedge clk);
        // Finish simulation
        repeat(5) @(posedge clk);
        $finish; end endmodule

```

